

## Set 1 Mark Scheme – Logic Gates & Control Systems

Q	Expanded Answer Guidance	Marks																				
1a	AND gate (accept: logical AND symbol, correct identification from diagram)	1																				
1b	<p>Base ideas:</p> <ul style="list-style-type: none"> <li>• Output is HIGH only when both inputs are HIGH</li> <li>• Output is 1 only if all inputs are 1</li> </ul> <p>Additional acceptable points:</p> <ul style="list-style-type: none"> <li>• If any input is 0 → output is 0</li> <li>• Behaves like multiplication in binary logic</li> <li>• Used where multiple conditions must be met simultaneously</li> <li>• Both switches must be closed (analogy accepted)</li> </ul>	2																				
1c	<table border="1" style="margin: auto;"> <thead> <tr> <th style="width: 33%;">A</th> <th style="width: 33%;">B</th> <th style="width: 33%;">Q</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">0</td> <td style="text-align: center;">0</td> <td style="text-align: center;">0</td> </tr> <tr> <td style="text-align: center;">0</td> <td style="text-align: center;">1</td> <td style="text-align: center;">1</td> </tr> <tr> <td style="text-align: center;">1</td> <td style="text-align: center;">0</td> <td style="text-align: center;">1</td> </tr> <tr> <td style="text-align: center;">1</td> <td style="text-align: center;">1</td> <td style="text-align: center;">1</td> </tr> </tbody> </table>	A	B	Q	0	0	0	0	1	1	1	0	1	1	1	1	2					
A	B	Q																				
0	0	0																				
0	1	1																				
1	0	1																				
1	1	1																				
2a	<ul style="list-style-type: none"> <li>• Inputs correctly labelled (A, B, etc.)</li> <li>• Output correctly labelled (Q/Y)</li> <li>• Direction of signal understood</li> </ul>	1																				
2b	<table border="1" style="margin: auto;"> <thead> <tr> <th style="width: 25%;">A</th> <th style="width: 25%;">B</th> <th style="width: 25%;">Q<sub>1</sub></th> <th style="width: 25%;">Q<sub>2</sub></th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">0</td> <td style="text-align: center;">0</td> <td style="text-align: center;">0</td> <td style="text-align: center;">1</td> </tr> <tr> <td style="text-align: center;">0</td> <td style="text-align: center;">1</td> <td style="text-align: center;">0</td> <td style="text-align: center;">1</td> </tr> <tr> <td style="text-align: center;">1</td> <td style="text-align: center;">0</td> <td style="text-align: center;">0</td> <td style="text-align: center;">1</td> </tr> <tr> <td style="text-align: center;">1</td> <td style="text-align: center;">1</td> <td style="text-align: center;">1</td> <td style="text-align: center;">0</td> </tr> </tbody> </table>	A	B	Q <sub>1</sub>	Q <sub>2</sub>	0	0	0	1	0	1	0	1	1	0	0	1	1	1	1	0	2
A	B	Q <sub>1</sub>	Q <sub>2</sub>																			
0	0	0	1																			
0	1	0	1																			
1	0	0	1																			
1	1	1	0																			
2c	NAND gate (accept: NOT-AND, inverted AND)	1																				
2d	<ul style="list-style-type: none"> <li>• AND gate combines A and B</li> <li>• NOT gate applied to C</li> <li>• OR gate combines both signals</li> </ul> <p>Accept:</p> <ul style="list-style-type: none"> <li>• Correct logic even if drawing style differs</li> <li>• Minor drawing errors if logic is clear</li> </ul>	3																				

3	<p>Band 1 (1–2):</p> <ul style="list-style-type: none"> <li>• Simple example (e.g. alarm OR switch)</li> <li>• Limited explanation</li> </ul> <p>Band 2 (3–4):</p> <ul style="list-style-type: none"> <li>• Clear example (e.g. safety system, machine start)</li> <li>• Explains OR = any input activates output</li> </ul> <p>Band 3 (5):</p> <ul style="list-style-type: none"> <li>• Strong engineering context (e.g. emergency stop, sensors)</li> <li>• Justifies why OR is appropriate</li> <li>• Links logic to real behaviour</li> </ul>	5
4a	<p>Open loop:</p> <ul style="list-style-type: none"> <li>• No feedback</li> <li>• Output not adjusted</li> <li>• Fixed operation</li> </ul> <p>Closed loop:</p> <ul style="list-style-type: none"> <li>• Uses feedback</li> <li>• Output is monitored</li> <li>• System self-corrects</li> </ul> <p>Accept:</p> <ul style="list-style-type: none"> <li>• Examples embedded in explanation</li> </ul>	4
4b	<p>Band 1 (1–2):</p> <ul style="list-style-type: none"> <li>• Basic example (e.g. toaster, timer)</li> </ul> <p>Band 2 (3–4):</p> <ul style="list-style-type: none"> <li>• Explains process and output</li> <li>• Mentions no feedback</li> </ul> <p>Band 3 (5–6):</p> <ul style="list-style-type: none"> <li>• Full system description (input → process → output)</li> <li>• Clearly states no feedback</li> <li>• Realistic engineering example</li> </ul>	6
5a	Closed-loop system (due to feedback from heat sensor)	1

5b	<p>Input:</p> <ul style="list-style-type: none"> <li>• Desired temperature / user setting</li> </ul> <p>Process:</p> <ul style="list-style-type: none"> <li>• Arduino processing signal</li> </ul> <p>Output:</p> <ul style="list-style-type: none"> <li>• Heating element / heat energy</li> </ul> <p>Feedback:</p> <ul style="list-style-type: none"> <li>• Heat sensor / temperature reading</li> </ul> <p>Controller:</p> <ul style="list-style-type: none"> <li>• Arduino / microcontroller</li> </ul>	2
5c	<p>Open-loop advantages:</p> <ul style="list-style-type: none"> <li>• Simple</li> <li>• Cheap</li> <li>• Fast response</li> <li>• Easy to maintain</li> </ul> <p>Closed-loop advantages:</p> <ul style="list-style-type: none"> <li>• Accurate</li> <li>• Self-correcting</li> <li>• Handles disturbances</li> <li>• Stable output</li> </ul> <p>Accept:</p> <ul style="list-style-type: none"> <li>• Comparative answers</li> <li>• Real-world examples</li> </ul>	5